

Tutorial 1

Problem 1

PROBLEM: Find the inverse Laplace transform of $F(s) = 10/[s(s+2)(s+3)^2]$.

Problem 2

PROBLEM: Find the ramp response for a system whose transfer function is

$$G(s) = \frac{s}{(s+4)(s+8)}$$

Problem 3

PROBLEM: Find the transfer function, $G(s) = V_o(s)/V_i(s)$, for each operational amplifier circuit shown in Figure P2.8. [Section: 2.4]



Problem 4

Solve the following differential equations

- a. $\frac{dx}{dt} + 7x = 5 \cos 2t$
- b. $\frac{d^2x}{dt^2} + 6\frac{dx}{dt} + 8x = 5 \sin 3t$
- c. $\frac{d^2x}{dt^2} + 8\frac{dx}{dt} + 25x = 10u(t)$

Assuming that the initial conditions for each part are as follows:

- (a) $x(0) = 4, x'(0) = -4;$
- (b) $x(0) = 4, x'(0) = 1;$
- (c) $x(0) = 2, x'(0) = 3$

Problem 5

Find the transfer function, $G(s) = V_L(s)/V(s)$, for each network shown in Figure P2.4. [Section: 2.4]

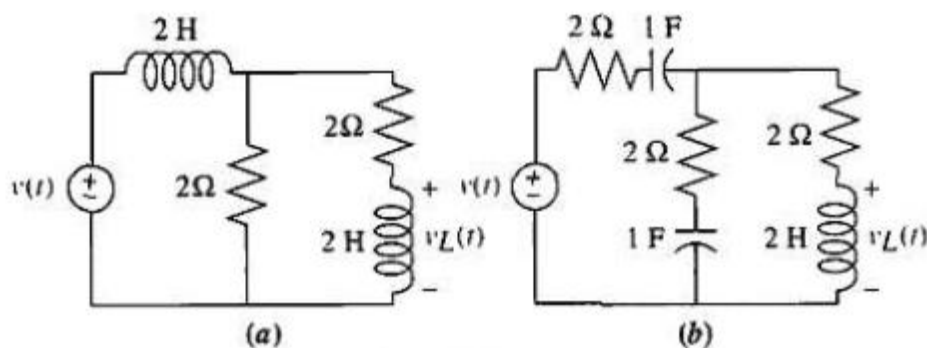


FIGURE P2.4